

CprE 381, Computer Organization and Assembly Level Programming

Lab 1 Report

Student Name Will Galles

Submit a typeset pdf version of this on Canvas by the due date. Refer to the highlighted language in the lab document for the context of the following questions.


[Part 1.c] Think of three more cases and record them in your lab report.

- Test Case 1 (Birthdate): Weight = 4, I_X = 5, I_Y = 5, O_Y should be 25, O_X should be 5.
- Test Case 2: Weight = 0, I_X = 5, I_Y = 10, O_Y should be 10, O_X should be 5
- Test Case 1: Weight = 3, I_X = 7, I_Y = 0, O_Y should be 21, O_X should be 7

[Part 1.e] For labels 1, 7, 22, and 28, specify where (VHDL file and line number) these values are located – some will be found in more than one place. Also attempt to explain the functionality of each label as it occurs in the code

- Label 1 corresponds with the entire TPU_MV_Element.vhd file, this points to the entire unit that contains and connects all of the smaller subcomponents.
- Label 7 corresponds with the instantiated adder g_Add1 on line 117 of the TPU_MV_Element.vhd file, this is the adder responsible for adding the carry input Y with the product of the weight and the X input.
- Label 22 corresponds with the Q output of the g_Weight load register module that is instantiated on line 92 of the TPU_MV_Element.vhd file, this register is responsible for loading the weight when the load signal is asserted. The Q output of this module is the weight that is stored in the register.
- Label 28 corresponds with the s_X1 that is defined on line 70 of the TPU_MV_Element.vhd file, this signal is used to map the output of the first delay of the X input to the input of the second delay of the X input. Routes between the output of the g_Delay1 module to the input of the g_Delay3 module.

 
[Part 1.g.v] In your lab report, include a screenshot of the waveform. Describe, in plain English, any differences between what you expected and what the simulation showed.




The output o_Y has a final value of 0x21 or 0d33 but it should have a final output value of 0x37 or 0d55. The final output o_X is correct in the case however.

[illegible]


[Part 3.a] Draw the truth table, Boolean equation, and Boolean circuit equivalent (using only two-input gates) that implements a 2:1 mux. Include this in your lab report.

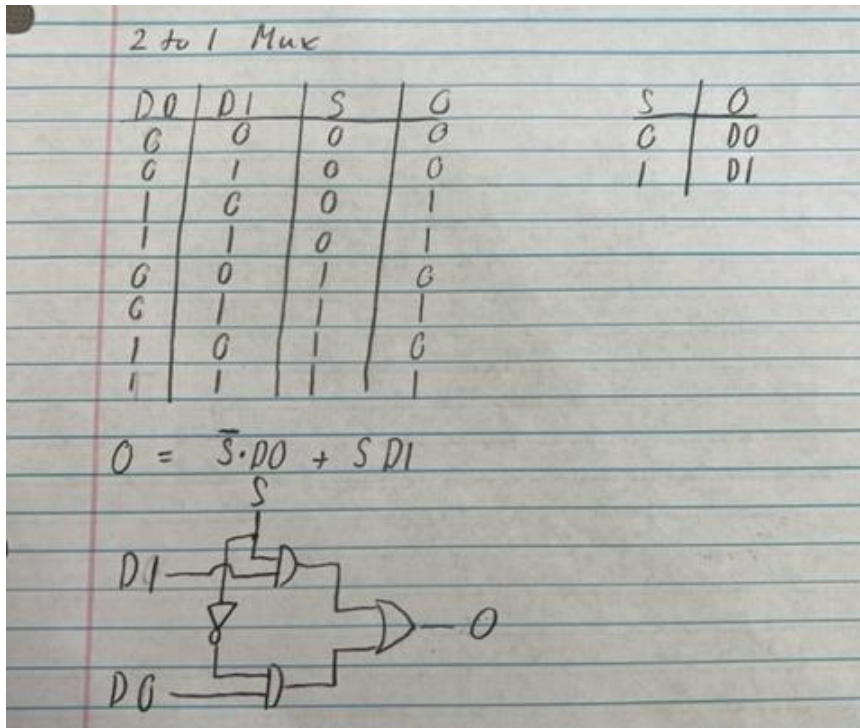


[Part 3.d] In your lab report, include a screenshot of the waveform. Make sure to label the screenshot with which module it is testing.

 


[Part 3.e] Again, in your lab report, include a labeled screenshot of the waveform showing the dataflow mux implementation working.

 


[Part 4] Include a waveform screenshot and corresponding description demonstrating it is working correctly.

 

 
[Part 5.b] Include a waveform screenshot and description in your lab report.




[Part 6.a] A full adder takes three single-bit inputs and produces two single-bit outputs – a sum and carry for the addition of the three input bits. Draw the truth table, Boolean equation, and Boolean circuit equivalent (using only two-input gates) that implements a 1-bit full adder. Include this in your report.

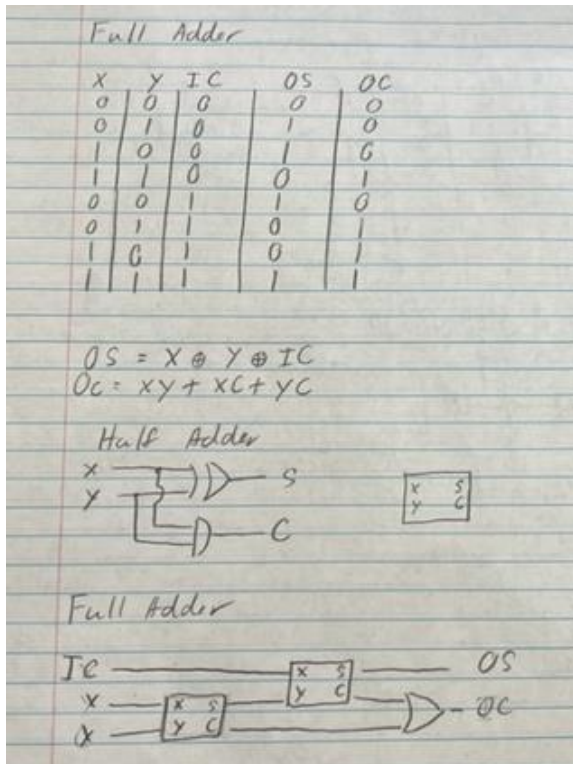

[Part 6.c] Then draw a schematic of the intended design, including inputs and outputs and at least the 0, 1, N-2, and N-1 stages. Include this in your report.

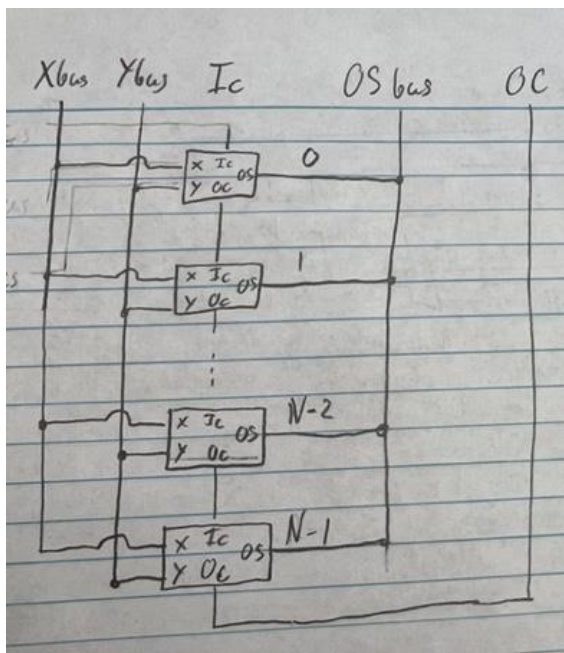

 [Part 6.d] Include an annotated waveform screenshot in your write-up.




First one is adding $0 + 0$ with a carry of 1 to get a total output of 1

Another is adding 0F0F0F0F and F0F0F0F0 with a carry bit so when the add together the sum clears and all is left is the carry


This last one is adding 11... and 22... for a result of 33...


[Part 7.a] Draw a schematic (don't use a schematic capture tool) showing how an N-bit adder/subtractor with control can be implemented using only the three main components designed in earlier parts of this lab (i.e., the N-bit inverter, N-bit 2:1 mux, and N-bit adder). How is the 'nAdd_Sub' bit used? Include this in your report.

The nAdd_Sub signal is both used to toggle between Y and inverted Y along with controlling the carry bit of the adder. Both of these together create a situation where you are either just adding both X and Y when the signal is low or adding X and 2's complement of Y when the signal is high. This addition of the 2's complement acts just the same as subtraction.

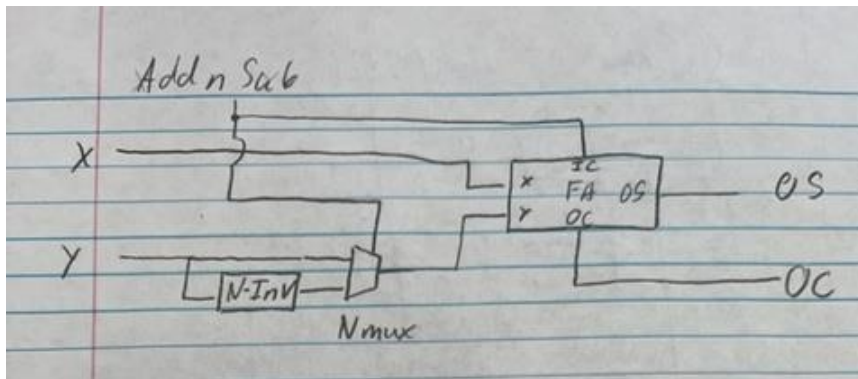

 [Part 7.c] Provide multiple waveform screenshots in your write-up to confirm that this component is working correctly. What test-cases did you include and why?



 

I chose my test cases to provide a good insight over the typical runtime for the adder along with some common edge cases. The first test was taking 0-0 which provided a output of 0 and a carry of 1. Next I added 0F0F0F0F + F0F0F0F0 which added up to FFFFFFFF. Next I calculated 33333333 - 11111111 for an answer of 22222222. Then I tested subtracting FFFFFFFF from it self for an answer of 0. Finally I did some smaller math problems like $22-37 = -15$, $37-22 = 15$ and $865 - 344 = 521$.